



# 數位**IC**設計

---

---

*Case Study*

# Case - Filter (1/8)

**FIR 滤波器**

**Filter tap=4**

$$y(n) = \sum_{m=0}^M h_m x(n-m)$$

output 和 前面4个输入有关

$$y(0) = h_0 x(0) + h_1 x(-1) + h_2 x(-2) + h_3 x(-3)$$

$$y(1) = h_0 x(1) + h_1 x(0) + h_2 x(-1) + h_3 x(-2)$$

$$y(2) = h_0 x(2) + h_1 x(1) + h_2 x(0) + h_3 x(-1)$$

$$y(3) = h_0 x(3) + h_1 x(2) + h_2 x(1) + h_3 x(0)$$

$$y(4) = h_0 x(4) + h_1 x(3) + h_2 x(2) + h_3 x(1)$$

**IIR**

output 现在 input 先前 input

$$y(n) - \sum_{m=1}^M k_m y(n-m) = \sum_{m=0}^M h_m x(n-m)$$



$$y(0) - [k_1 y(-1) + k_2 y(-2) + k_3 y(-3)] = h_0 x(0) + h_1 x(-1) + h_2 x(-2) + h_3 x(-3)$$

$$y(1) - [k_1 y(0) + k_2 y(-1) + k_3 y(-2)] = h_0 x(1) + h_1 x(0) + h_2 x(-1) + h_3 x(-2)$$

$$y(2) - [k_1 y(1) + k_2 y(0) + k_3 y(-1)] = h_0 x(2) + h_1 x(1) + h_2 x(0) + h_3 x(-1)$$

$$y(3) - [k_1 y(2) + k_2 y(1) + k_3 y(0)] = h_0 x(3) + h_1 x(2) + h_2 x(1) + h_3 x(0)$$
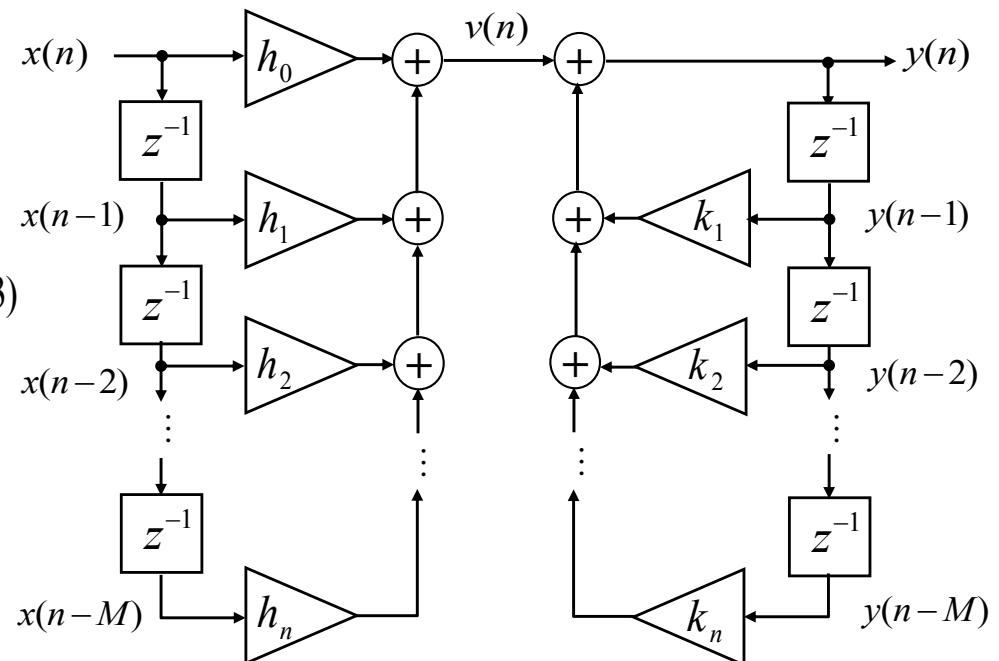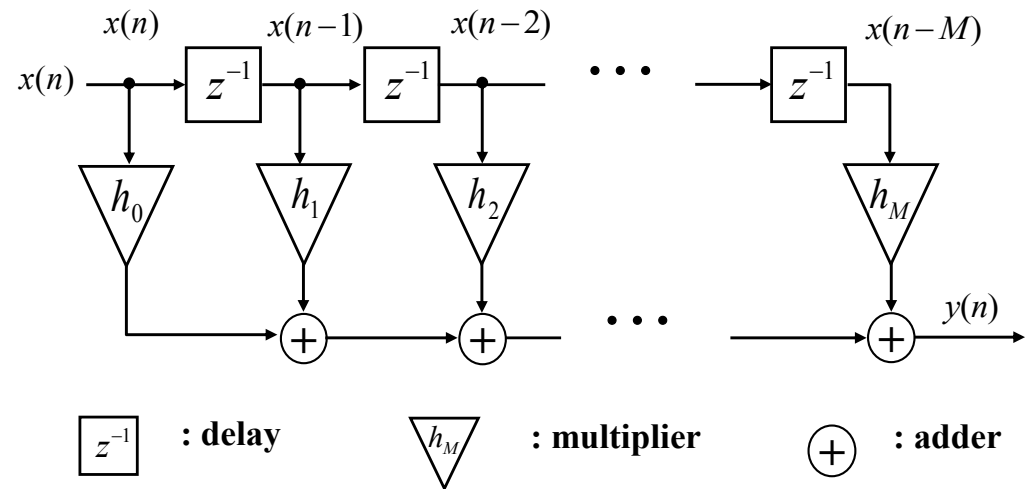
$$y(4) - [k_1 y(3) + k_2 y(2) + k_3 y(1)] = h_0 x(4) + h_1 x(3) + h_2 x(2) + h_3 x(1)$$




# Case - Filter (2/8)

tap=3


$h_0=2; h_1=4, h_2=6;$
 
```
module fir1(a, b, c, y);  
input [7:0] a, b, c;  
output [11:0] y;  
assign y = a*2+b*4+c*6;  
endmodule
```



```
module fir2(a, b, c, y);  
input [7:0] a, b, c;  
output [11:0] y;  
reg [11:0] y;  
always @(a or b or c)  
y = a*2+b*4+c*6;  
endmodule
```

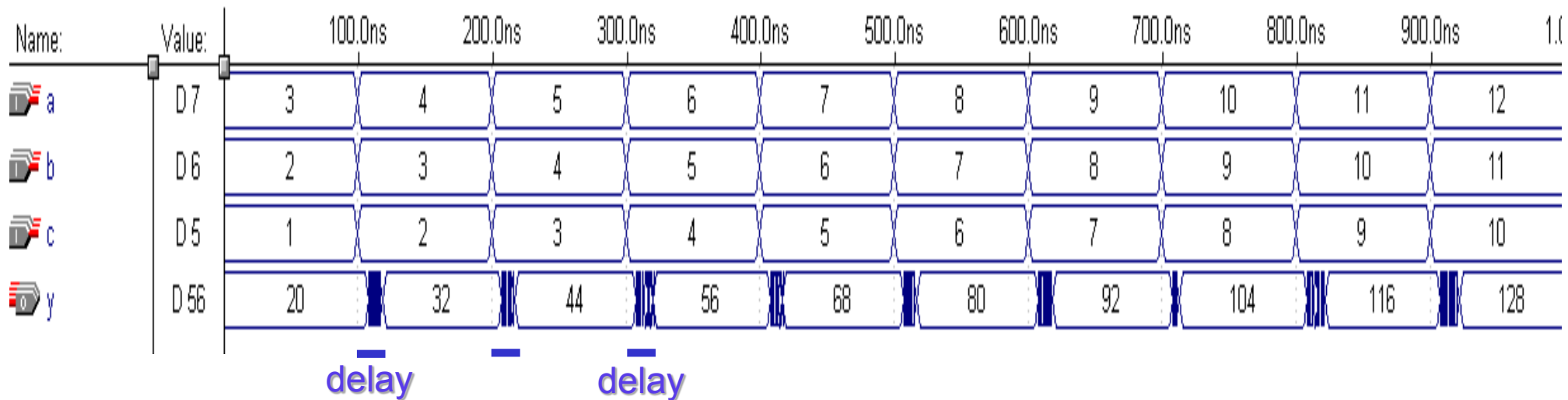Output: 20, 32, 44, 56, 68, 80, 92, 104, ....




# Case - Filter (3/8)

```

module fir3(a, b, c, y, ck);
input [7:0] a, b, c;
input ck;
output [11:0] y;
reg [11:0] y;
always @(posedge ck)
y = a*2+b*4+c*6;
endmodule

```

 


**Stable output**

Three inputs (a, b, c) must be entered concurrently (more pins, higher cost).

一次取3個input, 成本較高

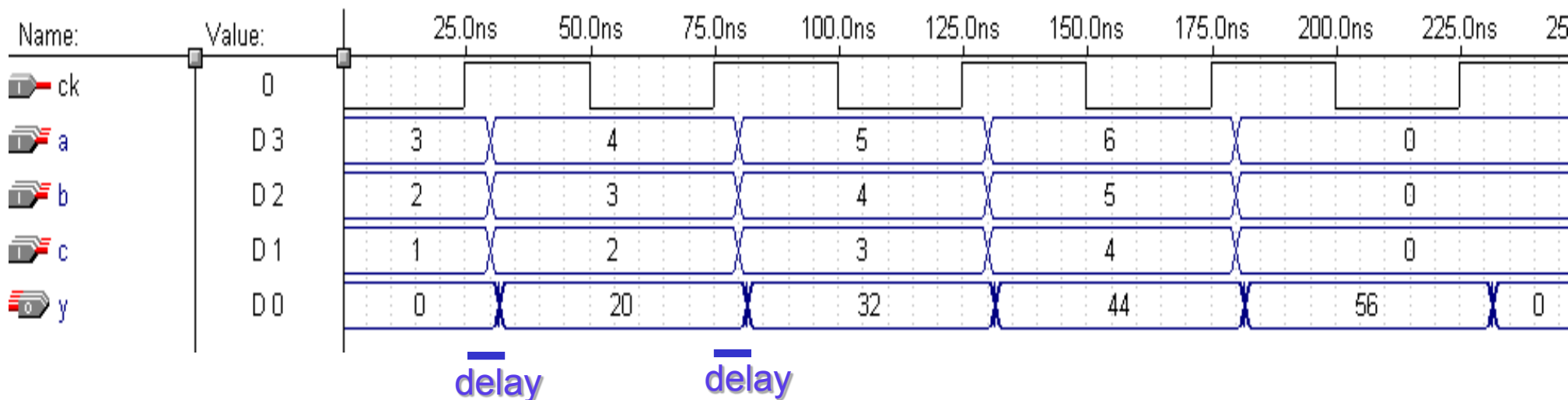Output: 20, 32, 44, 56, 68, 80, 92, 104, ....




The stable output is generated at the positive edge of clock.

## Case - Filter (4/8)


## fir2

## Unstable output

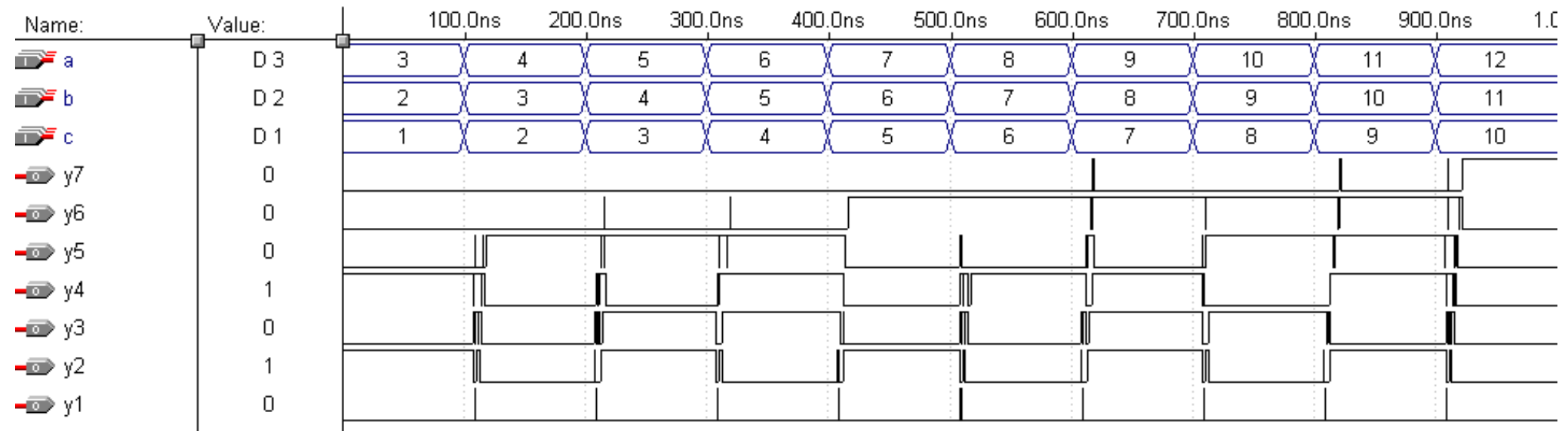

# fir3

## Stable output

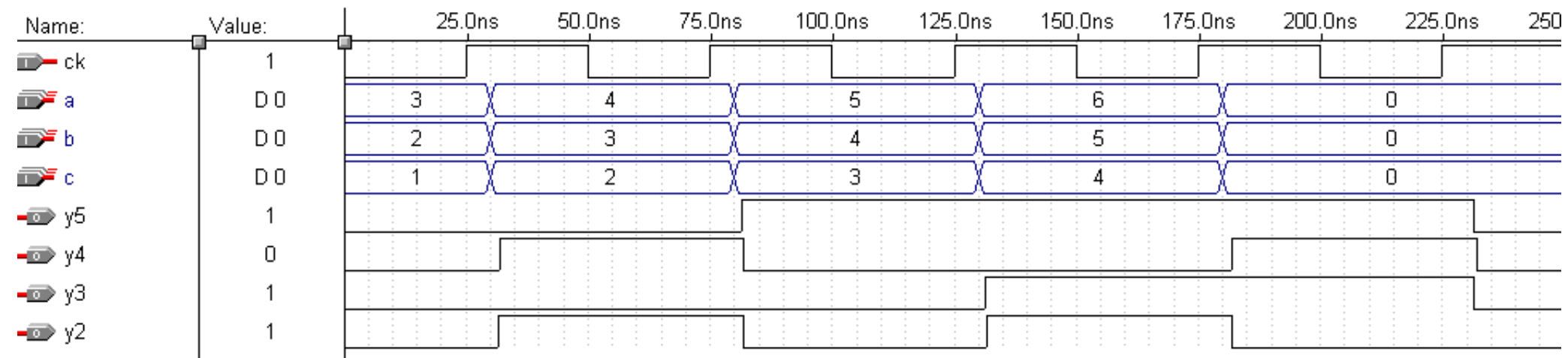

# Case - Filter (5/8)

```
module register(in, out, ck);
input [11:0] in;
input ck;
output [11:0] out;
reg [11:0] out;
always @(posedge ck)
out=in;
endmodule
```

```
`include "register.v"
module ffir1(in, out, ck);
input [11:0] in;
input ck;
output [11:0] out;
wire [11:0] x4, x3, x2, x1;
register r1(in, x3, ck);
register r2(x3, x2, ck);
register r3(x2, x1, ck);
register r4(x4, out, ck)
assign x4=x1*6+x2*4+x3*2;
endmodule
```


利用 reg, 當 clock 來的時候  
把上一時刻的值傳到下一個 reg  
⇒ 一次只需吃一個 input, 成本較低

```
module ffir1_a(in, out, ck);
input
input [11:0] in;
output [11:0] out;
reg [11:0] out;
reg [11:0] x4, x3, x2, x1;
always @(posedge ck)
begin
```

```
    x3<=in;
    x2<=x3;
    x1<=x2;
    out<=(x3*2+x2*4)+x1*6;
```

```
end
endmodule
```

 $T(n+1) \rightarrow 4$       3      2  
 $T(n) \rightarrow 3$       2      1 →




One input (in) is entered every clock cycle  
(more suitable for memory access and pins' cost)

# Case - Filter (6/8)


T(4)	→ 4	3	2
T(3)	→ 3	2	1
T(2)	→ 2	1	X
T(1)	→ 1	X	X
T(0)	→ X	X	X

To work well, every input must be ready before the positive edge of every clock

ffir1

 

 Output: 20, 32, 44, 56, 68, 80, 92, 104, ....




Correct results start here (4th clock), why ?
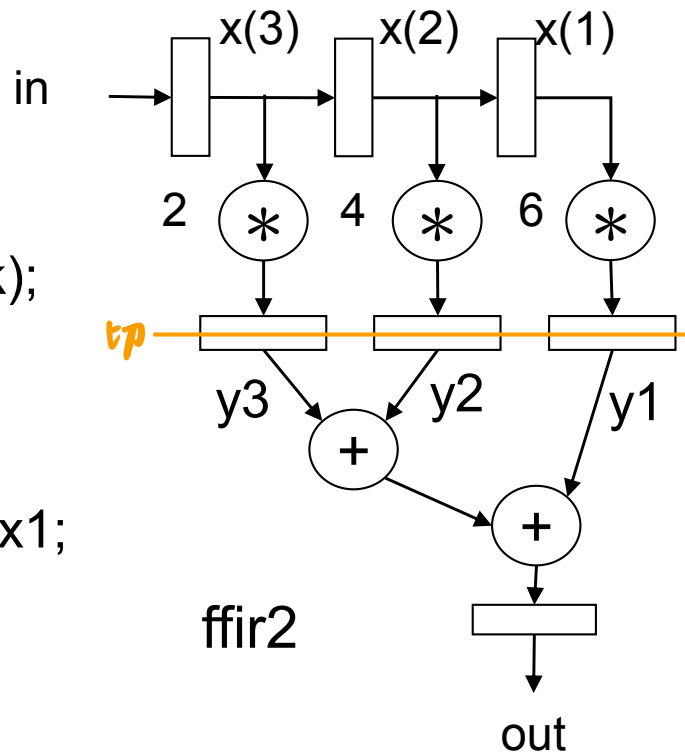
# Case - Filter (7/8)

```
`include "register.v"
module ffir2(in, out, ck);
input [11:0] in;
input ck;
output [11:0] out;
wire [11:0] x4, x3, x2, x1;
wire [11:0] t3, t2, t1;
wire [11:0] y3, y2, y1;
```

```
register r1(in, x3, ck); register r2(x3, x2, ck);
register r3(x2, x1, ck);
assign t3=x3*2; assign t2=x2*4; assign t1=x1*6;
register r4(t3, y3, ck); register r5(t2, y2, ck);
register r6(t1, y1, ck);
assign x4=y1+y2+y3;
register r7(x4, out, ck);
endmodule
```



## Datapath Pipelining

```
module ffir2_a(in, out, ck);
input      ck;
input [11:0] in;
output [11:0] out;
reg  [11:0] out;
reg  [11:0] x3, x2, x1;
reg  [11:0] y3, y2, y1;
always @(posedge ck)
begin
    x3<=in;
    x2<=x3;
    x1<=x2;
    y3<=x3*2;
    y2<=x2*4;
    y1<=x1*6;
    out<=(y3+y2)+y1;
end
endmodule
```




# Case - Filter (8/8)

T(4)	→ 4	3	2
T(3)	→ 3	2	1
T(2)	→ 2	1	X
T(1)	→ 1	X	X

Delay for \* is about 7.3 ns

Delay for register assign is about 6.1 ns


Delay for + is about 2.6 ns

 

Total delay = 7.3 + 6.1 = 13.4 ns (+ little wire delay)

Total delay = 2.6 \* 2 + 6.1 = 11.3 ns

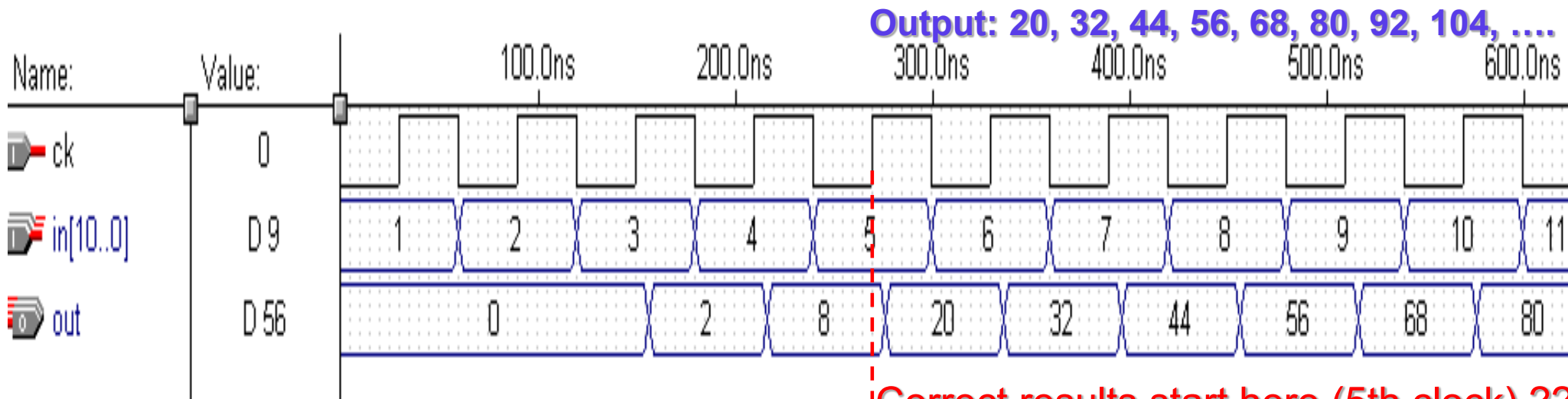Critical path = 13.4 ns => clock rate less than  $1/(13.4 \times 10^{-9}) \approx 74.6 \text{ MHz}$  軟快



Correct results start here (5th clock) ??

参考

心跳式阵列

# Case - Systolic Array (1/5)

## Systolic Array (FIR)

$$y(0) = h_0x(0) + h_1x(-1) + h_2x(-2) + h_3x(-3)$$



$$y(1) = h_0x(1) + h_1x(0) + h_2x(-1) + h_3x(-2)$$

$$y(2) = h_0x(2) + h_1x(1) + h_2x(0) + h_3x(-1)$$


$$y(3) = h_0x(3) + h_1x(2) + h_2x(1) + h_3x(0)$$

$$y(4) = h_0x(4) + h_1x(3) + h_2x(2) + h_3x(1)$$

 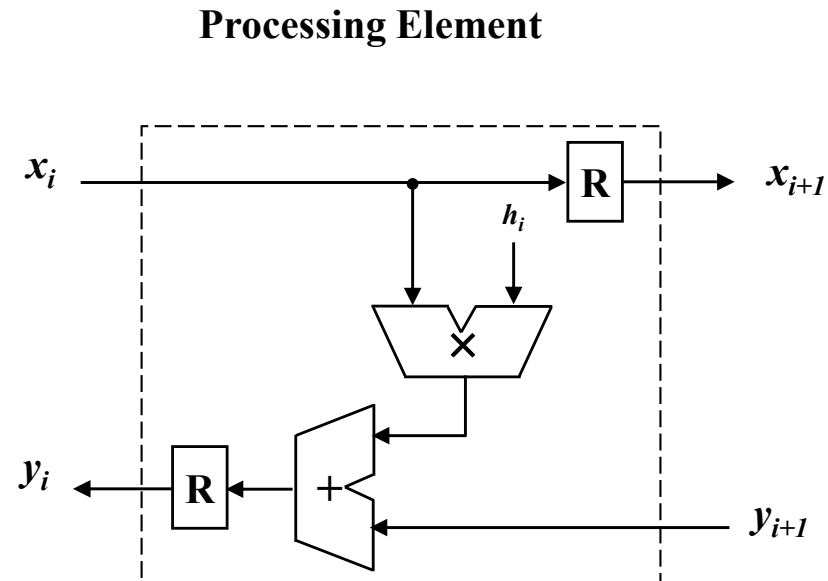+ : adder      × : multiplier  
 R : register     $h_i$  : coefficient



# Case - Systolic Array (2/5)

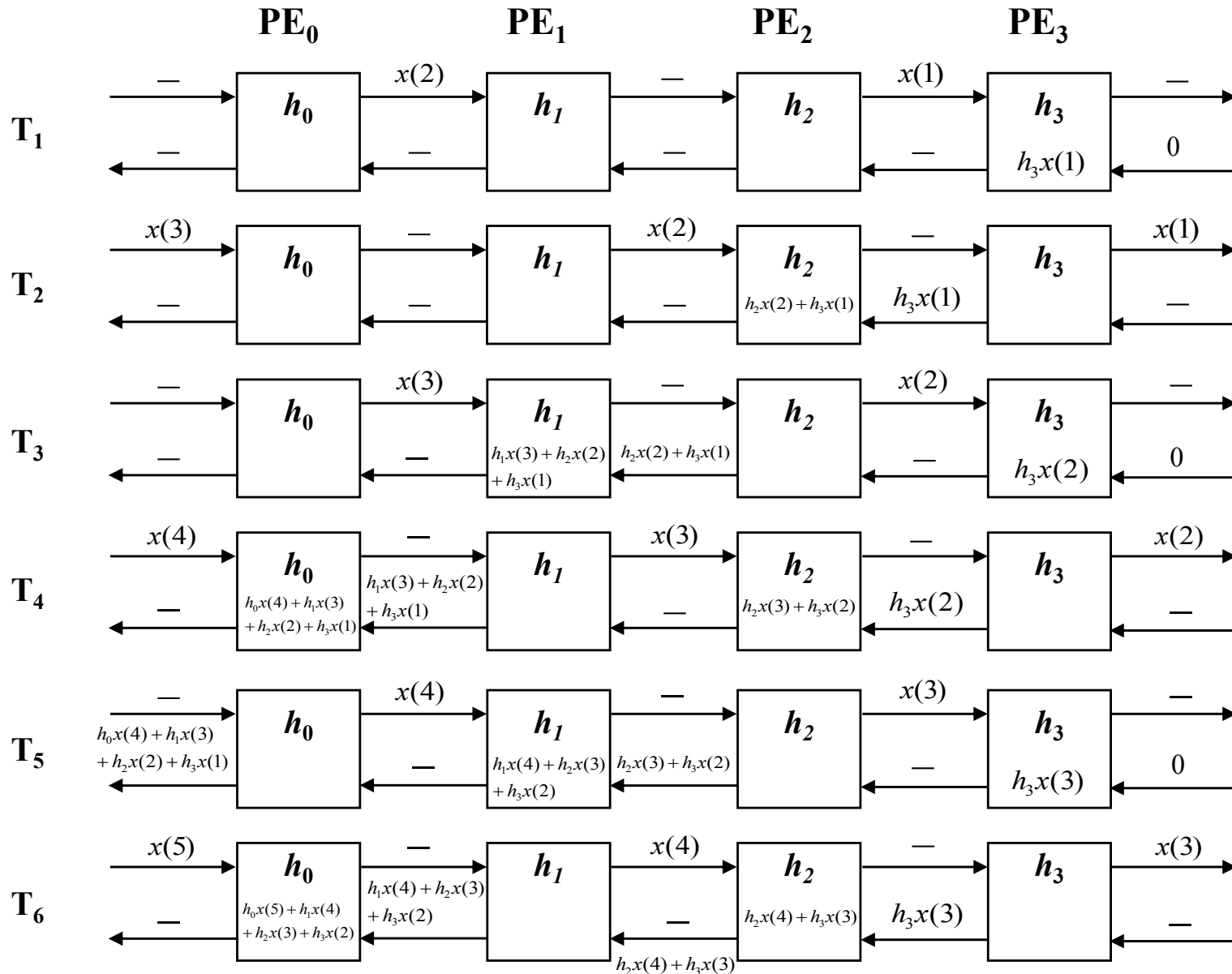


# Case - Systolic Array (3/5)

	$input\_x$	$pe0\_x$	$pe1\_x$	$pe2\_x$	$pe3\_x$	$pe4\_y$	$pe3\_y$	$pe2\_y$	$pe1\_y$	$output\_y$
$T_1$	—	$x(2)$	—	$x(1)$	—	—	—	—	—	—
$T_2$	$x(3)$	—	$x(2)$	—	$x(1)$	0	$h_3x(1)$	—	—	—
$T_3$	—	$x(3)$	—	$x(2)$	—	—	—	$h_2x(2) + h_3x(1)$	—	—
$T_4$	$x(4)$	—	$x(3)$	—	$x(2)$	0	$h_3x(2)$	—	$h_1x(3) + h_2x(2) + h_3x(1)$	—
$T_5$	—	$x(4)$	—	$x(3)$	—	—	—	$h_2x(3) + h_3x(2)$	—	$h_0x(4) + h_1x(3) + h_2x(2) + h_3x(1)$
$T_6$	$x(5)$	—	$x(4)$	—	$x(3)$	0	$h_3x(3)$	—	$h_1x(4) + h_2x(3) + h_3x(2)$	—
$T_7$	—	$x(5)$	—	$x(4)$	—	—	—	$h_2x(4) + h_3x(3)$	—	$h_0x(5) + h_1x(4) + h_2x(3) + h_3x(2)$

# Case - Systolic Array (4/5)
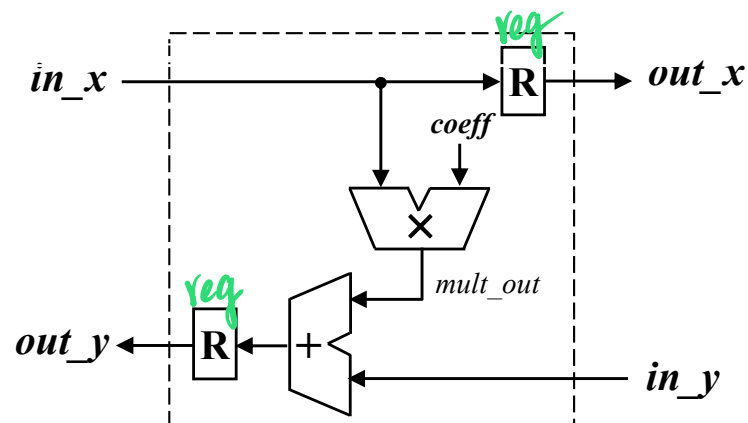
## Design\_1 structural

```
module pe(clk, reset, coeff, in_x, in_y, out_x, out_y);
parameter size = 8;
input  clk, reset;
input  [size-1:0]    in_x, coeff;
input  [size+size-1:0] in_y;
output [size-1:0]    out_x;
output [size+size-1:0] out_y;
wire  [size+size-1:0] mult_out, add_out;
reg_8 r1(clk, reset, in_x, out_x);
reg_16 r2(clk, reset, add_out, out_y);
assign mult_out = in_x * coeff;
assign add_out = mult_out + in_y;
endmodule
```




## behavior

```
module pe(clk, reset, coeff, in_x, in_y,
out_x, out_y);
parameter size = 8;
input      clk, reset;
input  [size-1:0]    in_x, coeff;
input  [size+size-1:0] in_y;
output [size-1:0]    out_x;
output [size+size-1:0] out_y;
reg  [size+size-1:0] out_y;
reg  [size-1:0]    out_x;

always@(posedge clk)
begin
    if(reset) begin
        out_x = 0;
        out_y = 0;
    end
    else begin
        out_y = in_y + (in_x * coeff);
        out_x = in_x;
    end
end
endmodule
```

# Case - Systolic Array (5/5)

 

```

/***** main *****/
module systolic(clk, reset, input_x, output_y);
parameter size = 8;
input clk, reset;
input [size-1:0] input_x;
output [size+size-1:0] output_y;
wire [size-1:0] pe0_x, pe1_x, pe2_x, pe3_x;
wire [size+size-1:0] pe1_y, pe2_y, pe3_y;

wire [size-1:0] h0 = 8'h01;
wire [size-1:0] h1 = 8'h01;
wire [size-1:0] h2 = 8'h01;
wire [size-1:0] h3 = 8'h01;
wire [size+size-1:0] pe4_y = 16'h0000;

pe pe_0(clk, reset, h0, input_x, pe1_y, pe0_x,
output_y);
pe pe_1(clk, reset, h1, pe0_x, pe2_y, pe1_x, pe1_y);
pe pe_2(clk, reset, h2, pe1_x, pe3_y, pe2_x, pe2_y);
pe pe_3(clk, reset, h3, pe2_x, pe4_y, pe3_x, pe3_y);
endmodule

```

```

/***** register_8bits *****/
module reg_8(clk, reset, in, out);
parameter size_in = 8;
input clk, reset;
input [size_in-1:0] in;
output [size_in-1:0] out;
reg [size_in-1:0] out;

always @(posedge clk)
begin
if(reset)
out=0;
else
out=in;
end
endmodule

```

```

/***** register_16bits *****/
module reg_16(clk, reset, in, out);
parameter size_in = 16;
input clk, reset;
input [size_in-1:0] in;
output [size_in-1:0] out;
reg [size_in-1:0] out;

always @(posedge clk)
begin
if(reset)
out=0;
else
out=in;
end
endmodule

```


# Case-Matrix Multiplication (1/2)

structural

## Matrix Multiplication

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} = \begin{bmatrix} c_{11} & c_{12} \\ c_{21} & c_{22} \end{bmatrix}$$

$$c = c + (a * b)$$

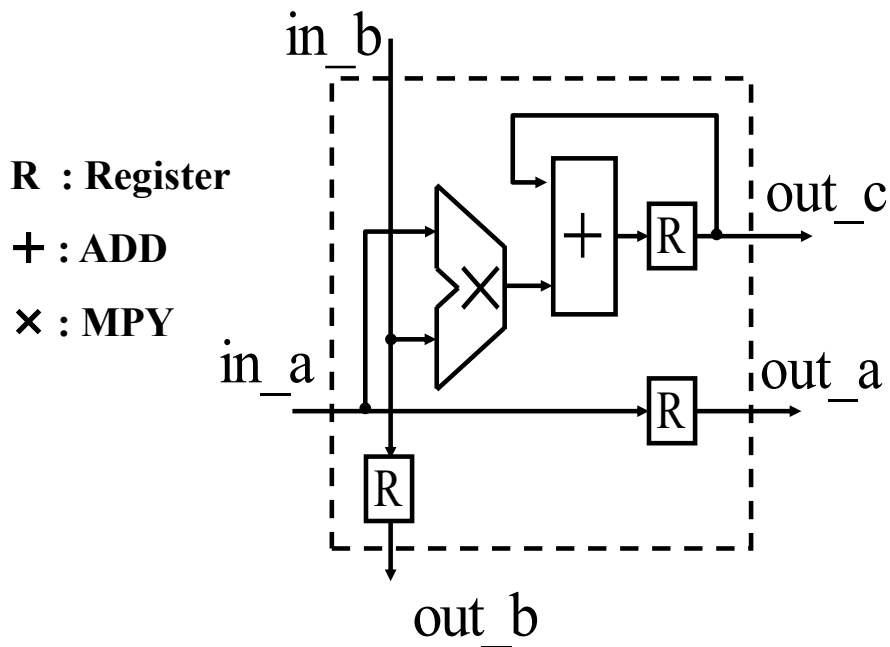

```
`include "reg_8.v"
```

```
`include "reg_16.v"
```

```
module PE(clk,reset,in_a,in_b,out_a,out_b,out_c);
```

```
parameter data_size=8;
```

```
input      reset,clk;
```

```
input      [data_size-1:0] in_a,in_b;
```

```
output     [data_size-1:0] out_a,out_b;
```

```
output     [2*data_size-1:0] out_c;
```

```
wire       [2*data_size-1:0] out_c,ADD_out,out_MPY;
```

```
wire       [data_size-1:0] out_a,out_b;
```

```
assign out_MPY=in_a*in_b;
```

```
assign ADD_out=out_MPY+out_c;
```

```
reg_16 reg_16_0(clk,reset,ADD_out,out_c);
```

```
reg_8 reg_delay_8_0(clk,reset,in_a,out_a);
```

```
reg_8 reg_delay_8_1(clk,reset,in_b,out_b);
```

```
endmodule
```

# Case-Matrix Multiplication (2/2)

## behavior

```
module PE_H(reset,clk,in_a,in_b,out_a,out_b,out_c);
```

```
parameter data_size=8;
```

```
input      reset,clk;
```

```
input      [data_size-1:0] in_a,in_b;
```

```
output     [2*data_size:0] out_c;
```

```
output     [data_size-1:0] out_a,out_b;
```

```
reg        [2*data_size:0] out_c;
```

```
reg        [data_size-1:0] out_a,out_b;
```

```
always @(posedge clk)
```

```
begin
```

```
  if(reset)
```

```
  begin
```

```
    out_a=0;
```

```
    out_b=0;
```

```
    out_c=0;
```

```
  end
```

```
  else
```

```
  begin
```

```
    out_c=out_c+in_a*in_b;
```


```
    out_a=in_a;
```

```
    out_b=in_b;
```

```
  end
```

```
end
```

```
endmodule
```

 

The rest of circuit can be designed easily....